

## Synchronous Languages—Lecture 07

Prof. Dr. Reinhard von Hanxleden

Christian-Albrechts Universität Kiel  
Department of Computer Science  
Real-Time Systems and Embedded Systems Group

7 May 2020

*Last compiled: May 7, 2020, 11:51 hrs*



### *Esterel V—The Constructive Circuit Semantics*

## The 5-Minute Review Session

1. What is the derivative (*Ableitung*) of a program?
2. How is the *program transition* of an Esterel program defined?
3. How do program transitions express logical coherence?
4. Which semantics for Esterel exist?
5. What are the *constructive coherence laws*, how do they differ from the logical coherence law?

## Overview

### The Circuit Semantics

Constructive circuits  
The basic circuit translation  
Translating the Esterel kernel

## Translating Esterel to Circuits

- ▶ Can consider Esterel programs as SW or HW descriptions
- ▶ As it turns out, the HW-equivalent of constructiveness is that the synthesized circuit is delay-independent
  - ▶ This gives a firm, physical base for the constructive semantics we just considered
- ▶ Can in turn simulate this synthesized HW-circuit in SW
  - ▶ This is just what the Esterel v5 compiler does
  - ▶ Can then also take advantage of HW optimization techniques
  - ▶ Use BDD-based techniques to check constructiveness

## Circuit Semantics—Introduction

```

module P1:
input I;
output O;
signal S1, S2 in
  present I then emit S1 end
||
  present S1 else emit S2 end
||
  present S2 then emit O end
end signal
end module

```

≡

```

circuit C1:
S1 = I
S2 = ¬S1
O = S2

```

- ▶ Resulting circuit is acyclic
- ▶ Hence always stabilizes
- ▶ Reactive and deterministic

## Circuit Semantics—Introduction

```

module P4:
output O;
present 0 then emit 0 end
end module

```

≡

```

circuit C4:
O = O

```

- ▶ Resulting circuit can stabilize at different values
- ▶ Not deterministic

## Circuit Semantics—Introduction

```

module P3:
output O;
present 0 else emit 0 end
end module

```

≡

```

circuit C3:
O = ¬O

```

- ▶ Resulting circuit never stabilizes
- ▶ Not reactive

## Circuit Semantics—Introduction

```

module P9:
[
  present 01 then emit 01 end
||
  present 01 then
    present 02 else emit 02 end
end
]

```


≡

```

circuit C9:
O1 = O1
O2 = O1 ∧ ¬O2


```

≡

 

- ▶ Reactive and deterministic
- ▶ But not constructive!


## Circuit Semantics—Introduction

 

- ▶ Reactive and deterministic
- ▶ **Meaning:** If it stabilizes, there is only one possible value for each wire's voltage
- ▶ **But:** Does it always stabilize?

## Circuit Semantics—Introduction

- ▶ Consider following delay assignment:

 

- ▶ Circuit is reactive and deterministic (Newtonian model)
- ▶ **But:** Circuit never stabilizes (Vibration model)
- ▶ **Hence: Electrical stabilization is not the conjunction of reactivity and determinism!**

This circuit can be expressed as

$$x(t) = x_1(t-1) \vee x_2(t-1)$$

with

$$x_1(t) = \neg x(t-1) \text{ and } x_2(t) = x(t-3),$$

resulting in

$$x(t) = \neg x(t-2) \vee x(t-4).$$

With  $x(t) = 0$  for  $t < 0$  this results in an oscillation of  $x$ , with period 2.

## Circuit Semantics—Introduction

```

module P13:
  present I then
    present O2 then emit O1 end
  else
    present O1 then emit O2 end
  end

```

≡

```

circuit C13:
  O1 = I ∧ O2
  O2 = ¬I ∧ O1

```

- ▶ Reactive and deterministic
- ▶ Cyclic, yet always stabilizes
- ▶ Hence: Electrical stabilization does not require acyclicity
- ▶ In fact: Electrical stabilization equivalent to constructiveness


## Constructive Circuits

## Constructive Boolean (intuitionistic) logic:

- ▶ Evaluate equations with constant folding rules
  - ▶ not 0 → 1
  - ▶ not 1 → 0
  - ▶ 1 or x → 1
  - ▶ x or 1 → 1
  - ▶ 0 or 0 → 0
  - ▶ 0 and x → 0
  - ▶ x and 0 → 0
  - ▶ 1 and 1 → 1
- ▶ There is no law of excluded middle (x or not x → 1)!
- ▶ Circuit equations yield solution iff circuit is delay insensitive (i.e., the original Esterel program is constructive)
  - ▶ Propagation of 1's corresponds to *Must*-analysis
  - ▶ Propagation of 0s corresponds to *Cannot*-analysis

## Constructive Circuits


## Basic building blocks

 

Z = X and Y



Z = X and not Y

 


Z = X or Y



Z = not(X or Y)



Z = X

 


Z = reg(X)

- ▶ Allow insertion of arbitrary delays
- ▶ Registers:
  - ▶  $reg(X) = 0 \rightarrow pre(X)$

## The Basic Circuit Translation

- ▶ Structural translation
- ▶ Follows state semantics
  - ▶ Associate registers with “1” statements (pause)
  - ▶ Associate combinational logic with all other statements
  - ▶ Build up program-circuit from subcircuits
  - ▶ Additional boot register to implement initial state
- ▶ Basic circuit translation does not address schizophrenia (see later)


## Interface for subcircuits

 

## Inputs:


- ▶ **GO**: Starts statement afresh
- ▶ **RES**: Resumes execution of a selected statement
- ▶ **SUSP**: Suspend execution of the statement
  - ▶ Registers keep their current value unless killed because of the KILL input
- ▶ **KILL**: Unsets statement's registers in case of a trap exit

## Interface for subcircuits contd.

 

- ▶ **E** and **E'**: input/output signal interface
- ▶ Are compound pins or buses
  - ▶ Contain one elementary pin per signal visible in the scope of the current statement.
- ▶ May freely extract specific signals  $s$  or  $s'$  out of  $E$  or  $E'$ .
- ▶ As for the  $K$  pins, the  $E'$  pins are explicitly unset when the statement is not executed
  - ▶ I.e. when  $\neg(\text{GO} \vee (\text{RES} \wedge \text{SEL}))$


## Interface for subcircuits contd.

 

## Outputs:

- ▶ **SEL**: Indicates that a state in statement is currently selected for resumption, i.e. that some internal pause register is set
  - ▶ Is simply the disjunction of the internal registers.
- ▶ **K0, K1, ...**: Completion codes (1-hot encoding)

## The Global Environment

 

- ▶ Boot register sets GO input in initial instant
- ▶ At each clock cycle
  - ▶ set RES
  - ▶ clock the registers


- ▶ Note that the initial 1 for RES does no harm, as no register is selected yet
- ▶ SEL and K1 are not needed globally
- ▶ The output signals are also fed back to the input signals—as if they were declared as signals at the top-level (see signal declaration later)

## Translating the Esterel Kernel

- ▶ Completion, with  $k \neq 1$ :



- ▶  $k = 1$  (pause):

 


Use these conventions to simplify diagrams:

- ▶ Unused inputs are not pictured.
- ▶ Not all outputs are pictured. An omitted output is assumed to be explicitly unset, i.e. to be driven by a 0 constant


## Translating the Esterel Kernel

▶ !s:

 


## Translating the Esterel Kernel

▶  $s? p, q$ :

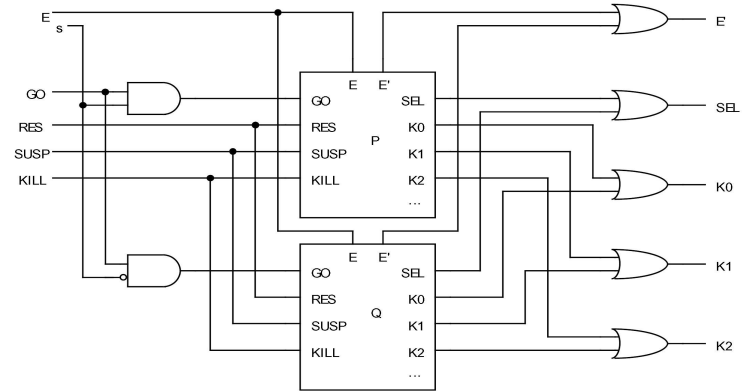


## Translating the Esterel Kernel

▶  $p; q$ :

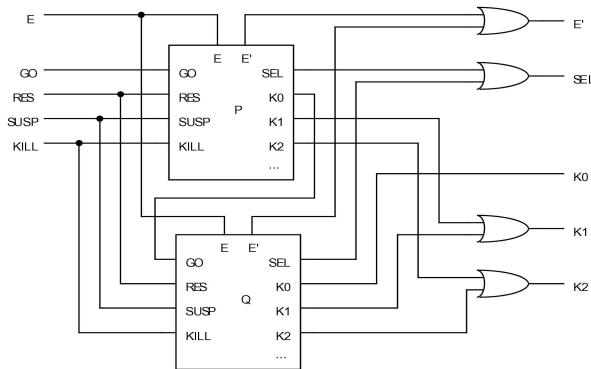


## Translating the Esterel Kernel

▶  $s \supset p$ :

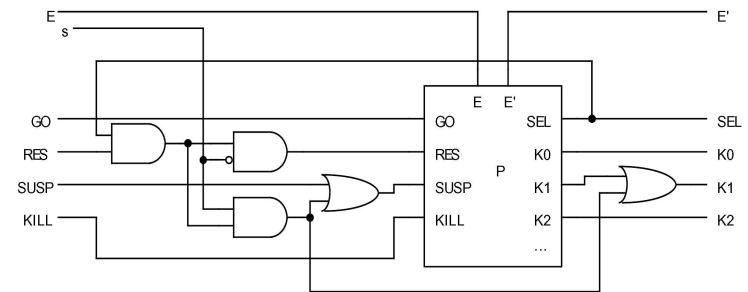

## Translating the Esterel Kernel


►  $p^*$ :

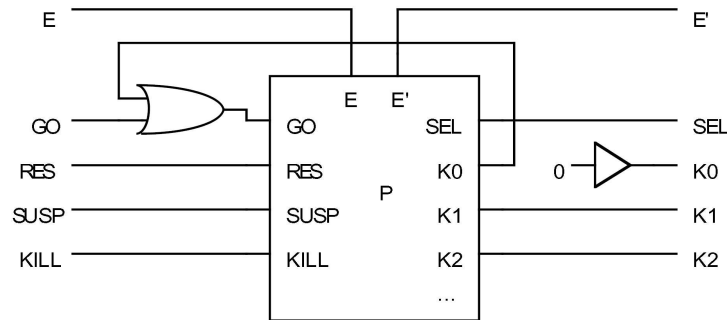
 
## Translating the Esterel Kernel


►  $p \parallel q$  (contd):

- The synchronizer computes the maximum of the completion codes
- Implemented with this (constructive) circuit:



## Translating the Esterel Kernel

►  $p \parallel q$ :

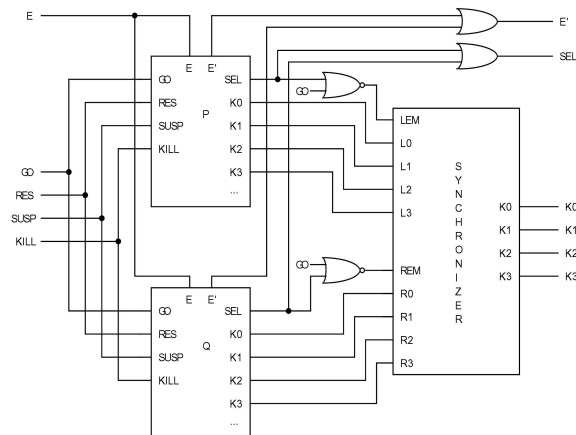


- The inputs LEM and REM indicate the case where the sets of completion codes are empty—which is the case if neither GO is set nor one of the internal registers




## Translating the Esterel Kernel

▶  $\{p\}$ :

 


## Translating the Esterel Kernel

▶  $p \setminus s$ :

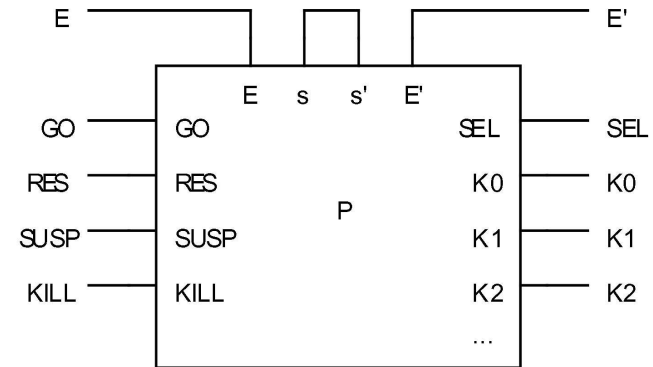


## Translating the Esterel Kernel

▶  $\uparrow p$ :

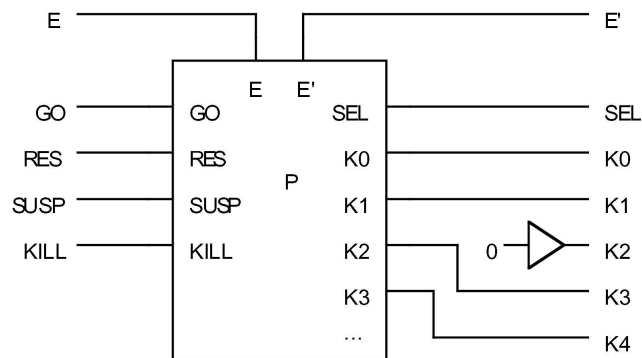

## Example

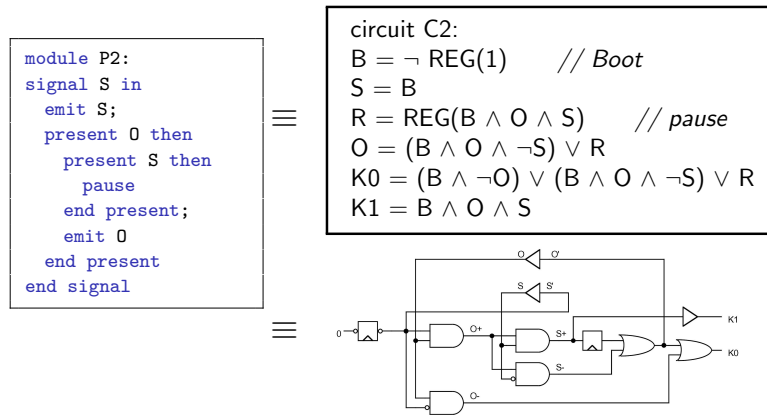

Can you find the bug in the diagram?

- ▶ (Hint: have a look at the O- gate)

When evaluating this, it turns out that in the initial instant, it is

- ▶  $B = S = 1$
- ▶  $R = O = 0$
- ▶  $K0 = 1$ —hence this terminates after the first instance
- ▶  $K1 = 0$ —as expected, as  $K0$  already evaluated to 1

## To Go Further

- ▶ Gérard Berry, The Constructive Semantics of Pure Esterel, Draft book, current version 3.0, Dec. 2002, Chapters 10 and 11, <http://www-sop.inria.fr/members/Gerard.Berry/Papers/EsterelConstructiveBook.zip>