

# Synchronous Languages—Lecture 07

Prof. Dr. Reinhard von Hanxleden

Christian-Albrechts Universität Kiel  
Department of Computer Science  
Real-Time Systems and Embedded Systems Group

21 Nov. 2016

*Last compiled: November 21, 2016, 10:00 hrs*



*Esterel V—The Constructive  
Circuit Semantics*

## The 5-Minute Review Session

1. What is the derivative (*Ableitung*) of a program?
2. How is the *program transition* of an Esterel program defined?
3. How do program transitions express logical coherence?
4. Which semantics for Esterel exist?
5. What are the *constructive coherence laws*, how do they differ from the logical coherence law?

# Overview

## The Circuit Semantics

Constructive circuits

The basic circuit translation

Translating the Esterel kernel

## Translating Esterel to Circuits

- ▶ Can consider Esterel programs as SW or HW descriptions
- ▶ As it turns out, the HW-equivalent of constructiveness is that the synthesized circuit is delay-independent
  - ▶ This gives a firm, physical base for the constructive semantics we just considered
- ▶ Can in turn simulate this synthesized HW-circuit in SW
  - ▶ This is just what the Esterel v5 compiler does
  - ▶ Can then also take advantage of HW optimization techniques
  - ▶ Use BDD-based techniques to check constructiveness

## Circuit Semantics—Introduction

```
module P1:  
  input I;  
  output O;  
  signal S1, S2 in  
    present I then emit S1 end  
  ||  
    present S1 else emit S2 end  
  ||  
    present S2 then emit O end  
end signal  
end module
```

≡

```
circuit C1:  
  S1 = I  
  S2 = ¬S1  
  O = S2
```

- ▶ Resulting circuit is acyclic
- ▶ Hence always stabilizes
- ▶ Reactive and deterministic

# Circuit Semantics—Introduction

```
module P3:  
  output 0;  
  present 0 else emit 0 end  
end module
```

 $\equiv$ 

```
circuit C3:  
  0 = ¬0
```

- ▶ Resulting circuit never stabilizes
- ▶ Not reactive

# Circuit Semantics—Introduction

```
module P4:  
  output 0;  
  present 0 then emit 0 end  
end module
```

 $\equiv$ 

```
circuit C4:  
  0 = 0
```

- ▶ Resulting circuit can stabilize at different values
- ▶ Not deterministic

## Circuit Semantics—Introduction

```


module P9:
[
  present 01 then emit 01 end
||
  present 01 then
    present 02 else emit 02 end
end
]

```

≡

circuit C9:  
 $O1 = O1$   
 $O2 = O1 \wedge \neg O2$

≡

 

- ▶ Reactive and deterministic
- ▶ But not constructive!




# Circuit Semantics—Introduction

```
module P12:  
  present 0 then  
    emit 0;  
  else  
    emit 0  
  end
```

≡

```
circuit C12:  
  0 = 0 ∨ ¬0
```


≡

 

- ▶ Reactive and deterministic
- ▶ **Meaning:** If it stabilizes, there is only one possible value for each wire's voltage
- ▶ **But:** Does it always stabilize?

## Circuit Semantics—Introduction

- ▶ Consider following delay assignment:

 

- ▶ Circuit is reactive and deterministic (Newtonian model)
- ▶ **But:** Circuit never stabilizes (Vibration model)
- ▶ **Hence: Electrical stabilization is not the conjunction of reactivity and determinism!**

# Circuit Semantics—Introduction

```
module P13:  
  present I then  
    present O2 then emit O1 end  
  else  
    present O1 then emit O2 end  
end
```

 $\equiv$ 

```
circuit C13:  
O1 = I ∧ O2  
O2 = ¬I ∧ O1
```

- ▶ Reactive and deterministic
- ▶ Cyclic, yet always stabilizes
- ▶ **Hence:** Electrical stabilization does not require acyclicity
- ▶ **In fact:** Electrical stabilization equivalent to constructiveness

# Constructive Circuits

## Basic building blocks



$Z = X \text{ and } Y$



$Z = X \text{ and not } Y$



$Z = X \text{ or } Y$



$Z = \text{not}(X \text{ or } Y)$



$Z = X$



$Z = \text{reg}(X)$

- ▶ Allow insertion of arbitrary delays
- ▶ Registers:
  - ▶  $\text{reg}(X) = 0 \rightarrow \text{pre}(X)$

## Constructive Circuits


### Constructive Boolean (intuitionistic) logic:

- ▶ Evaluate equations with constant folding rules
  - ▶ not 0  $\rightarrow$  1
  - ▶ not 1  $\rightarrow$  0
  - ▶ 1 or x  $\rightarrow$  1
  - ▶ x or 1  $\rightarrow$  1
  - ▶ 0 or 0  $\rightarrow$  0
  - ▶ 0 and x  $\rightarrow$  0
  - ▶ x and 0  $\rightarrow$  0
  - ▶ 1 and 1  $\rightarrow$  1
- ▶ There is no law of excluded middle ( $x$  or not  $x \rightarrow 1$ )!
- ▶ Circuit equations yield solution iff circuit is delay insensitive (i.e., the original Esterel program is constructive)
  - ▶ Propagation of 1's corresponds to *Must*-analysis
  - ▶ Propagation of 0s corresponds to *Cannot*-analysis

# The Basic Circuit Translation

- ▶ Structural translation
- ▶ Follows state semantics
  - ▶ Associate registers with “1” statements (pause)
  - ▶ Associate combinational logic with all other statements
  - ▶ Build up program-circuit from subcircuits
  - ▶ Additional boot register to implement initial state
- ▶ Basic circuit translation does not address schizophrenia (see later)


## Interface for subcircuits

 

### Inputs:

- ▶ **GO**: Starts statement afresh
- ▶ **RES**: Resumes execution of a selected statement
- ▶ **SUSP**: Suspend execution of the statement
  - ▶ Registers keep their current value unless killed because of the KILL input
- ▶ **KILL**: Unsets statement's registers in case of a trap exit

## Interface for subcircuits contd.

 


## Outputs:

- ▶ **SEL**: Indicates that a state in statement is currently selected for resumption, i.e. that some internal pause register is set
  - ▶ Is simply the disjunction of the internal registers.
- ▶ **K0, K1, ...**: Completion codes (1-hot encoding)




## Interface for subcircuits contd.

 

- ▶ E and E': input/output signal interface
- ▶ Are compound pins or buses
  - ▶ Contain one elementary pin per signal visible in the scope of the current statement.
- ▶ May freely extract specific signals  $s$  or  $s'$  out of E or E'.
- ▶ As for the K pins, the E' pins are explicitly unset when the statement is not executed
  - ▶ I.e. when  $\neg( GO \vee ( RES \wedge SEL))$



# The Global Environment

 


- ▶ Boot register sets GO input in initial instant
- ▶ At each clock cycle
  - ▶ set RES
  - ▶ clock the registers

## Translating the Esterel Kernel

- Completion, with  $k \neq 1$ :

  


- $k = 1$  (pause):

 


# Translating the Esterel Kernel


▶ !s:

 

## Translating the Esterel Kernel

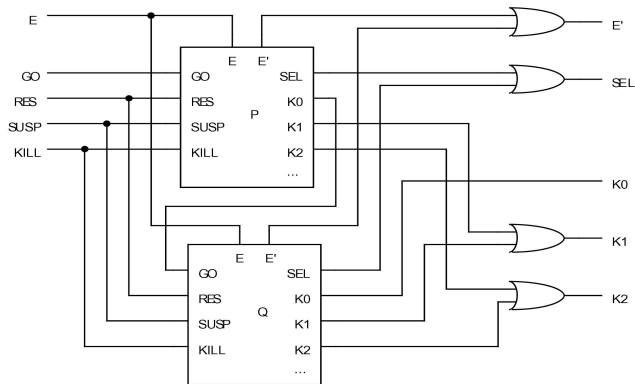
▶  $p; q$ :

## Translating the Esterel Kernel

 
▶  $s?p, q:$ 

## Translating the Esterel Kernel

▶  $s \supset p$ :

 


## Translating the Esterel Kernel

 ▶  $p^*$ :




## Translating the Esterel Kernel

 
▶  $p \parallel q$ :
 
# Translating the Esterel Kernel


- ▶  $p \parallel q$  (contd):
  - ▶ The synchronizer computes the maximum of the completion codes
  - ▶ Implemented with this (constructive) circuit:




## Translating the Esterel Kernel

 ▶  $\{p\}$ :

## Translating the Esterel Kernel

 ▶  $\uparrow p$ :

## Translating the Esterel Kernel

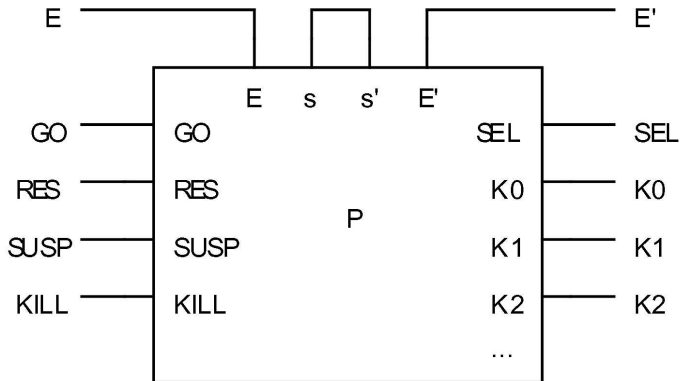▶  $p \setminus s$ :


## Example

```

module P2:
  signal S in
    emit S;
    present 0 then
      present S then
        pause
      end present;
    emit 0
  end present
end signal

```

circuit C2:

  $B = \neg \text{REG}(1)$  // *Boot* $S = B$  $R = \text{REG}(B \wedge O \wedge S)$  // *pause* $O = (B \wedge O \wedge \neg S) \vee R$  $K0 = (B \wedge \neg O) \vee (B \wedge O \wedge \neg S) \vee R$  $K1 = B \wedge O \wedge S$ 

## To Go Further

- ▶ Gérard Berry, The Constructive Semantics of Pure Esterel, Draft book, current version 3.0, Dec. 2002, Chapters 10 and 11,  
<http://www-sop.inria.fr/members/Gerard.Berry/Papers/EsterelConstructiveBook.zip>